
ECE 205: LAB 4

NE555 TIMER AND RC CIRCUITS

UNIVERSITY OF ILLINOIS AT URBANA-CHAMPAIGN
DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING

AUTHORS

NATHAN GLASER JOSEPH SPECHT
NGLASER3 JSPECHT3

PROFESSOR

JONATHON SCHUH

JULY 14, 2024

Contents

1	Statement of Purpose	1
2	PreLab Deliverables	1
3	Procedure	2
4	Observation and Data	3
5	Analysis	4
6	Conclusions	4
7	Appendix	4

1 Statement of Purpose

The purpose of this lab was to characterize the NE555 integrated circuit and determine how it works. We accomplished this goal utilizing the ubiquitous program LTspice.

2 PreLab Deliverables

For the first prelab deliverable, we created the NE555 circuit with operating parameters of $R_1 = R_2 = 1\text{ k}\Omega$, $C = 0.5\text{ }\mu\text{F}$, and $V_{cc} = 9\text{ V}$. By using the following equations given in the Texas Instruments 555 manual, we were able to calculate the period to be 1.03972 ms .

$$t_H = \ln(2) \cdot (R_1 + R_2) C = 0.69315\text{ms} \quad (1)$$

$$t_L = \ln(2) \cdot (R_2) C = 0.34657\text{ms} \quad (2)$$

$$\text{period} = T = t_H + t_L = \ln(2) \cdot (R_1 + 2R_2) C \quad (3)$$

Equipped with the period, we then sketched the waveform for the output voltage and the capacitor voltage, which is given as follow:

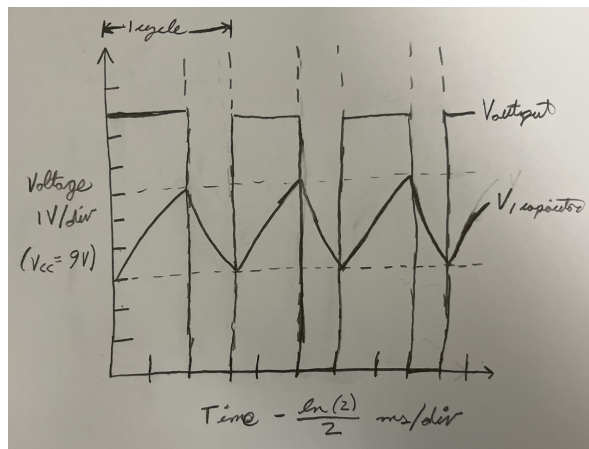


Figure 1: Voltage Waveform Sketch for NE555 Integrated Circuit

For the second pre-lab deliverable, we assumed a "full cycle" refers to a period. Under this *modus operandi*, if we want at least two full cycles displayed on the oscilloscope, we know two periods $2T = 2.07944\text{ ms}$ will be fully pictured with a timebase of 0.5 ms .

3 Procedure

To begin, we constructed a circuit with the NE555 timer as the centerpiece. We then added 2 resistors, R_1 and R_2 , and two capacitors, C_1 and C_2 . Further we added a voltage source. R_2 had a constant resistivity of $1\text{ k}\Omega$, while R_1 had a resistivity of $1\text{ k}\Omega$ for the first trial and $2\text{ k}\Omega$ for the second. The two capacitors, C_1 and C_2 , had capacitances of $.5$ and $.01\text{ }\mu\text{F}$ capacitance, respectively. Finally the voltage source had a strength of 9 V . The schematic we used to complete this lab is presented below in Fig. 2.

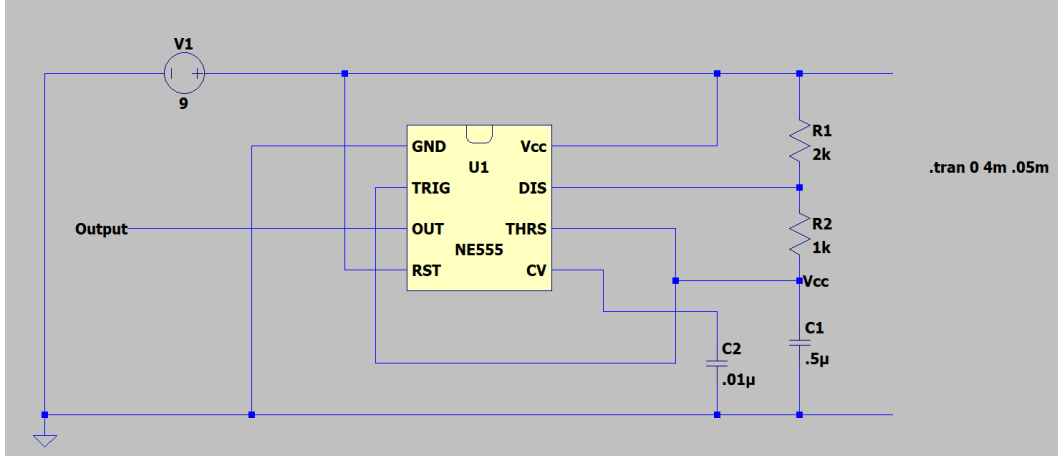


Figure 2: Schematic of circuit modeled in LTspice

We conducted two trials, the first with R_1 set to $1\text{ k}\Omega$ and then $2\text{ k}\Omega$ for the second. For both trials we ran a transient simulation spanning 4 ms , with 0.05 ms time-steps. From these simulations we output the voltage at node V_{cc} and at node *Output*.

4 Observation and Data

From our first trial, with the resistivity of R_1 set to $1\text{ k}\Omega$, we produced the plot presented in Fig 3.

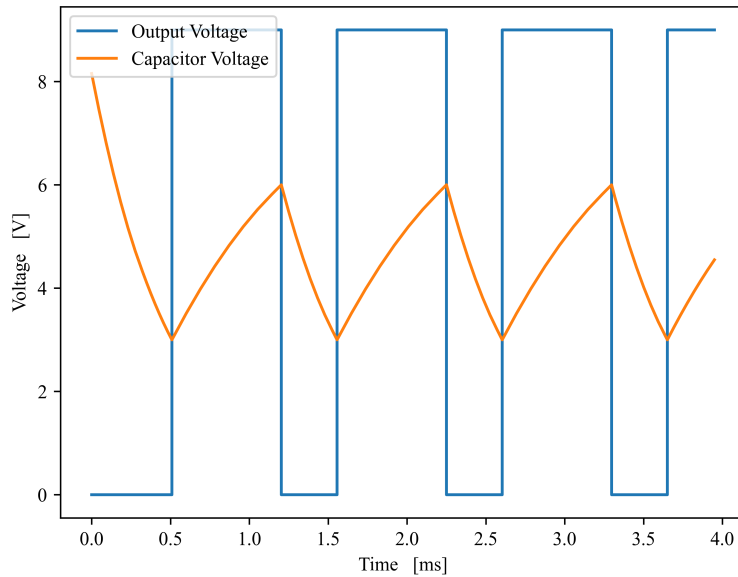


Figure 3: *Output* and V_{cc} voltage, R_1 set to $1\text{ k}\Omega$

Next, from our second trial, where the resistivity of R_1 was set to $2\text{ k}\Omega$, we constructed Fig. 4.

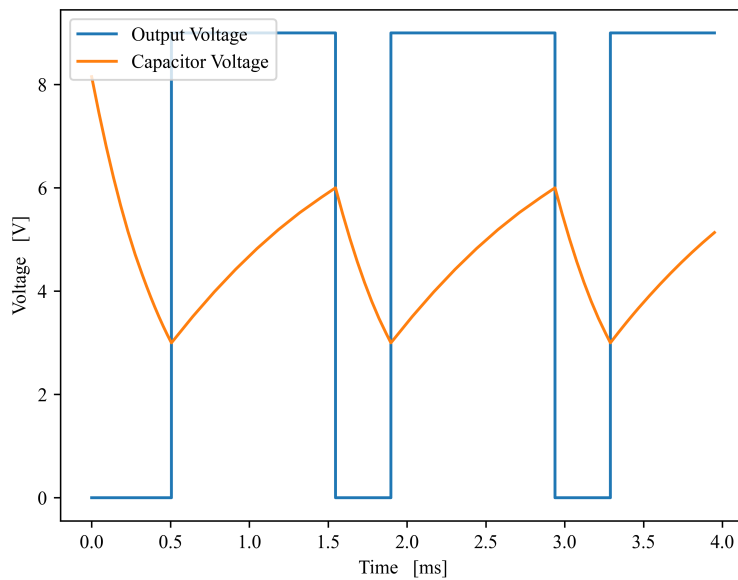


Figure 4: *Output* and V_{cc} voltage, R_1 set to $2\text{ k}\Omega$

5 Analysis

From Figs. 3 and 4, the dependencies of the the charging and discharging regions can be ascertained as follows: the discharging period **is not** dependent on the resistivity of R_1 , while the charging period **is** dependent on the resistivity of R_1 . The discharge time in the first trial is 0.35362, and the discharge time of the second trial is 0.35131; a negligible difference. The charging time of the first trial is 0.69377, where the charging time of the second trial was 1.04065.

6 Conclusions

In conclusion, the charging time depends only on R_2 and the discharging time depends on both R_1 and R_2 .

7 Appendix

All output files and schematic screenshots are in [this](#) Google Drive folder. r1k refers to the output file of the first trial, and r2k is that of the second trial.