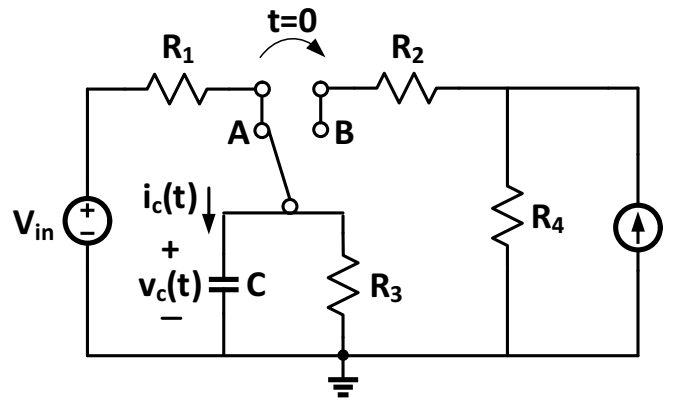


Name:

UIN:

1. The switch in the circuit shown below is moved at time $t = 0$ as shown. Compute voltage $v_c(t)$ and current $i_c(t)$ after the switch is moved. Assume $R_1 = 2 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$, $R_3 = 2 \text{ k}\Omega$, $R_4 = 4 \text{ k}\Omega$, $C = 1 \text{ }\mu\text{F}$, $V_{\text{in}} = 10 \text{ V}$, $I = 6 \text{ mA}$.



2. The switch in the circuit shown below is moved at time $t = 0$ as shown. Compute voltage $v_c(t)$ after the switch is moved. Assume $R_1 = 1 \text{ k}\Omega$, $R_2 = 1 \text{ k}\Omega$, $R_3 = 1 \text{ k}\Omega$, $R_4 = 1 \text{ k}\Omega$, $C = 1 \text{ }\mu\text{F}$, $V_{in1} = 8 \text{ V}$, and $V_{in2} = 4 \text{ V}$.

