

---

---

# ECE 205: LAB 6

## FILTERS AND OP-AMPS

---

---

*UNIVERSITY OF ILLINOIS AT URBANA-CHAMPAIGN*  
*DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING*

### **AUTHORS**

NATHAN GLASER    JOSEPH SPECHT

NGLASER3    JSPECHT3

### **PROFESSOR**

JONATHON SCHUH

JULY 31, 2024

# Contents

<b>1</b>	<b>Statement of Purpose</b>	<b>1</b>
<b>2</b>	<b>PreLab Deliverables</b>	<b>1</b>
<b>3</b>	<b>Procedure</b>	<b>2</b>
<b>4</b>	<b>Observation and Data</b>	<b>3</b>
<b>5</b>	<b>Analysis</b>	<b>4</b>

# 1 Statement of Purpose

The purpose of this lab is to gain familiarity with filters and OP-AMPs, and how they pertain to voltage regulation.

## 2 PreLab Deliverables

For the first prelab deliverable, we investigated the left side of the given circuit, which is encapsularized in the left box of the picture below:

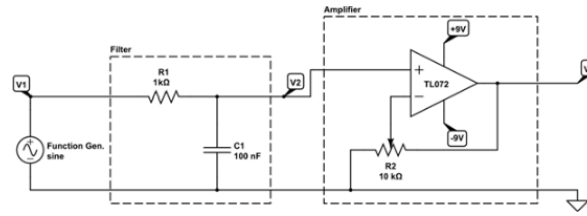


Figure 1: Circuit Diagram

For this circuit, the cutoff frequency is given as:

$$\omega_C = \frac{1}{RC} = \frac{1}{(1k\Omega)(100nF)} = 10,000 \frac{rad}{s} = \frac{10,000}{2\pi} Hz \quad (1)$$

and this filter is a low pass filter.

### 3 Procedure

To begin, to complete challenge 1 we constructed the simple circuit shown in Fig. 2. With this circuit we simulated the output voltage, the voltage at the top right corner node, as a function of the ac voltage frequency.

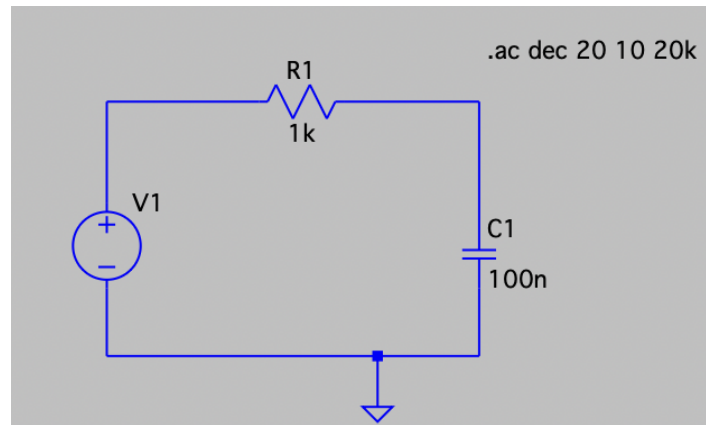


Figure 2: Schematic of challenge 1 circuit in LTspice

Next, to complete challenge 2 we constructed the much more complex circuit presented in Fig. 3. With this circuit we simulated the output and input voltage to the amplifier as a function of time. With this plot we are able to visualize the amplifier gain, and changing the resistance of  $R_{2,1}$  and  $R_{2,2}$  we can see the cut-off amplitude.

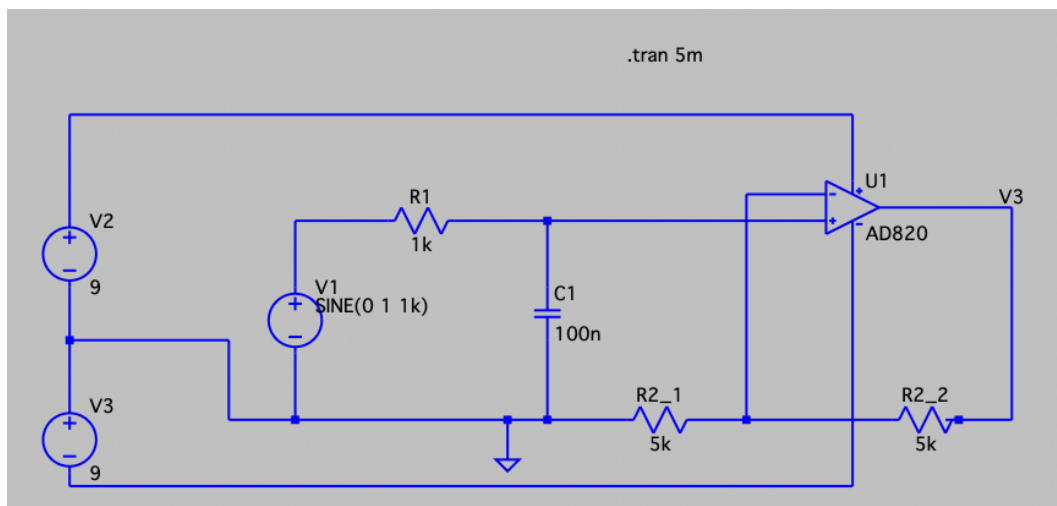


Figure 3: Schematic of challenge 2 circuit in LTspice

## 4 Observation and Data

For challenge 1, we output the voltage of the top-right node as a function of ac frequency. This is presented in Fig. 4.

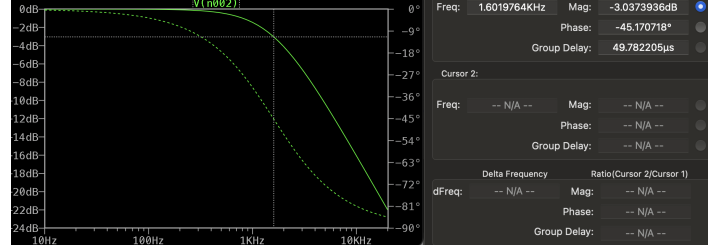


Figure 4: Output voltage of the filter section of the circuit

To continue we outputted the input and output voltage to the amplifier as a function of time, with  $R_{2.1} = R_{2.2} = 5 \text{ k}\Omega$ . This is presented in Fig. 5. Further, through trial and error, we found the cutoff amplitude to be achieved when  $R_{2.1} = 0.93 \Omega$  and  $R_{2.2} = 9.07 \Omega$ . This cutoff amplitude is presented in Fig. 6.

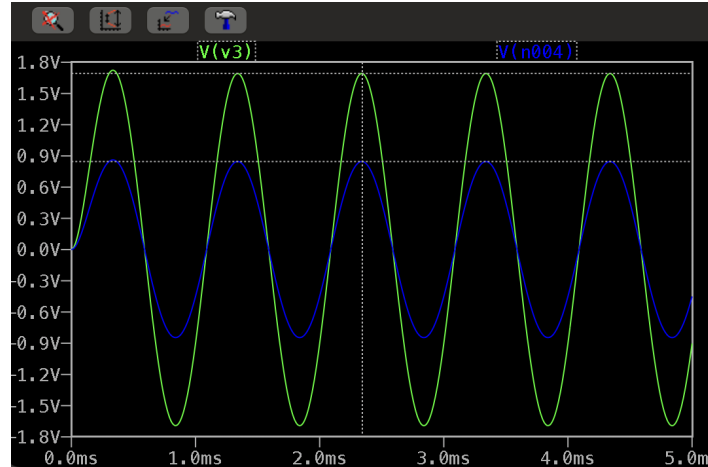


Figure 5: Amplitude of  $V_{in}$  and  $V_{out}$  for  $R_{2.1} = R_{2.2}$

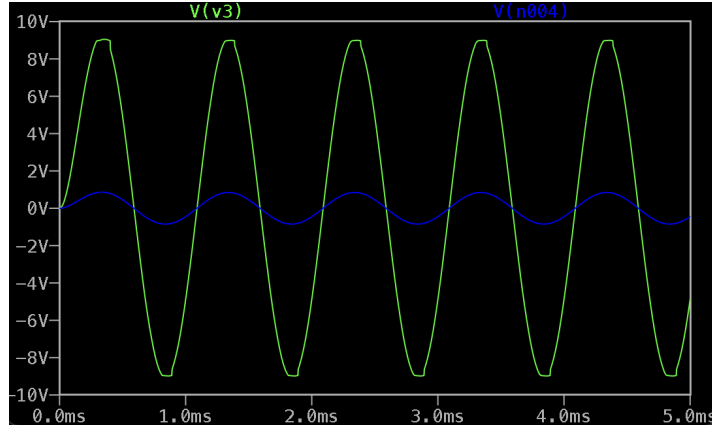


Figure 6: Amplitude of  $V_{in}$  and  $V_{out}$  for  $R_{2,1} = 0.93 \, \Omega$  and  $R_{2,2} = 9.07 \, \Omega$

## 5 Analysis

The observed gain in Fig. 5 is 2, which conveniently pops out of the equation for gain, Eq. 2, when inserting  $5 \, \text{k}\Omega$  for both resistance values. Further, when inserting the resistances from the second part of challenge 2, we obtain an output voltage of  $9 \, \text{V}$ .

$$V_{out} = V_{in} \cdot \left(1 + \frac{R_2}{R_1}\right) \quad (2)$$